

# 6-Channel Temperature Monitor & Logger

Measures from  
-240 °C to +850 °C

By **Clemens Valens** (Elektor Labs) and **Sunil Malekar** (India)

Temperature is an important parameter to control in many industrial processes. At home, too, the fridge, freezer, heater, kitchen oven, and air conditioner all measure and adjust the temperature to get their job done. Weather stations, cars, computers, tablets and smartphones keep an eye on temperature too. Come to think of it, temperature may well be the world's most surveyed physical quantity.

Even my low-cost Bluetooth speaker sounds an alarm when it gets too hot (as I discovered after placing it on a heater). Because humankind likes to measure temperature so much, we decided to design a device capable of measuring up to six of them. Usually, thermometers only measure one temperature — some can do two, often labelled 'inside' and 'outside' — but for process control more channels may be required. Range is also important, which is why the device presented here can measure temperatures across the massive range from -240 °C


up to +850 °C. Note that these are software limits; the real-world limits greatly depend on the sensors being used.


### Resistance thermometers

To measure temperature, we will use so-called RTDs in the shape of Pt100 probes. RTD is short for Resistance Temperature Detector, a device consisting of a length of metal wire with a known resistance/temperature relationship spiralled on a suitable supporting material. The metal typically used is platinum, copper or

nickel. Sensor precision depends on the purity of the metal. Platinum has the most stable resistance/temperature relationship over the largest temperature range.

 A Pt100 probe is an RTD made from platinum wire ('Pt' in the Periodic Table). The value '100' indicates that its resistance is 100 Ω at 0 °C. Other values can be



 

had too, like 500, 1000 or even 2000. Pt100 sensors are widely used and easy to find. They come in different quality grades — classes — that determine their price, range,

accuracy and precision. They also come with a variable number of connecting wires: 2, 3 or 4. The extra wires are used to measure the resistance of

## PROJECT DECODER



8051  
temperature monitoring



entry level  
→ intermediate level  
expert level



4 hours approx.



soldering iron,  
C2 programmer (see text)



£45 / €50 / \$55 approx.

### Quick Features

- 6 channels for Pt100 RTDs
- Range: -240 °C to +850 °C
- 8051 MCU
- 2-line alphanumeric display
- Serial data output in CSV format

 


Figure 1: The relationship (in blue) between resistance and temperature of a platinum (Pt) wire is nonlinear. It may be approximated using a lookup table of short “straight” segments of the curve.

 


Figure 2: The Howland current source has a very high output impedance. It is used here to excite a 3-wire RTD.


the RTD’s connecting wires (more on that later). As these wires — that can be rather long — behave like inaccurate RTDs, it is important to compensate the sensor for them to ensure reliable and repeatable results. To avoid complicating our system too much, we opted for 3-wire RTDs.

### An RTD is not a thermocouple

This is important to understand. A thermocouple is a junction of two different metals that produces a temperature-dependent voltage as a result of the thermoelectric (Seebeck) effect. Therefore, a thermocouple does not need a power source to operate whereas an RTD requires some form of excitation. Thermocouples tend to be less precise than RTDs, but they are very cheap.
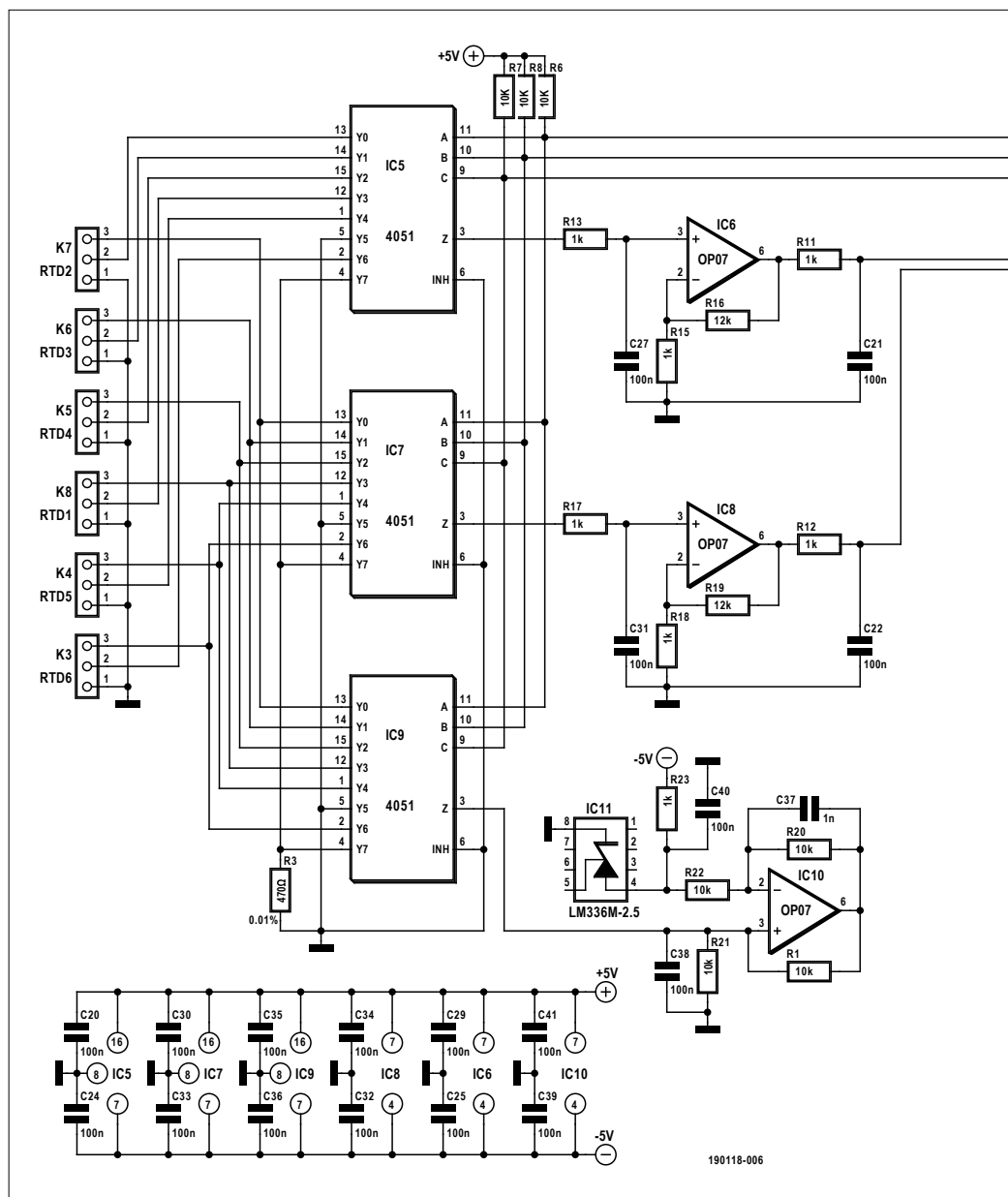
### Linearity

One last but important thing to mention about RTDs is their slightly non-linear resistance/temperature relationship (see **Figure 1**). This implies that some calculations must be done to obtain the correct temperature from the measured resistance. The Callendar–Van Dusen equation has long been used for platinum RTDs, but in 1990 the *Comité International des Poids et Mesures* replaced it by a 12<sup>th</sup>-order polynomial valid over the temperature range from -259.35 °C to 0 °C and a second, 9<sup>th</sup>-order polynomial for temperatures from 0 °C up to 961.78 °C. Because evaluating such polynomials calls for heaps of computing power (and debugging), most applications simply use lookup tables. We did so too.



## Howland current source

As briefly mentioned above, an RTD must be excited in some way to make it usable. Either a constant voltage or a constant current source can be used for this. We preferred a constant current source since it poses fewer problems with long sensor wires. In this case the voltage across the sensor depends on the current only and, of course, the temperature, and not on the resistance of the connecting wires in addition.

Constant current source designs are plentiful but a popular one for use with RTDs is the Howland current source or current pump (Figure 2). This kind of source has the advantage of having a very high output impedance compared to other current source designs and it can sink as well as source current. However,

to make it work as intended, resistors R1 to R4 surrounding the opamp should have a tolerance of 1% or better.

When the ratio R1/R2 is equal to the ratio R3/R4, then the output current is given by:

$$I_{RTD} = (V^+ - V^-) / R3 \text{ [A]}$$

## Compensating for connecting wires

Figure 2 also shows how the RTD is connected to the current source with its three wires. Assuming that the three wires are identical and that we can measure the voltages 'V' and 'V<sub>RW</sub>' at a very high input impedance (meaning that there is no current flowing in the directions of V and V<sub>RW</sub> (properly:  $V_{RW}$ ), then the voltage across the RTD is given as:

$$V_{RTD} = V - 2 V_{RW} \text{ [V]}$$

This completes our theoretical introduction, and we can move on to studying the actual schematic.

## The input multiplexer

Looking at the left of Figure 3, we find connectors K3–K8 for the six RTD channels. One wire of each RTD is connected to GND, the two others to a Type 4051 CMOS multiplexer IC. IC7 forwards the signal 'V' from Figure 2 to the rest of the system; IC5 does the same for signal 'VRW'. The third multiplexer, IC9, works the other way around and connects the output of the current source — constructed around IC10 — to the selected RTD.

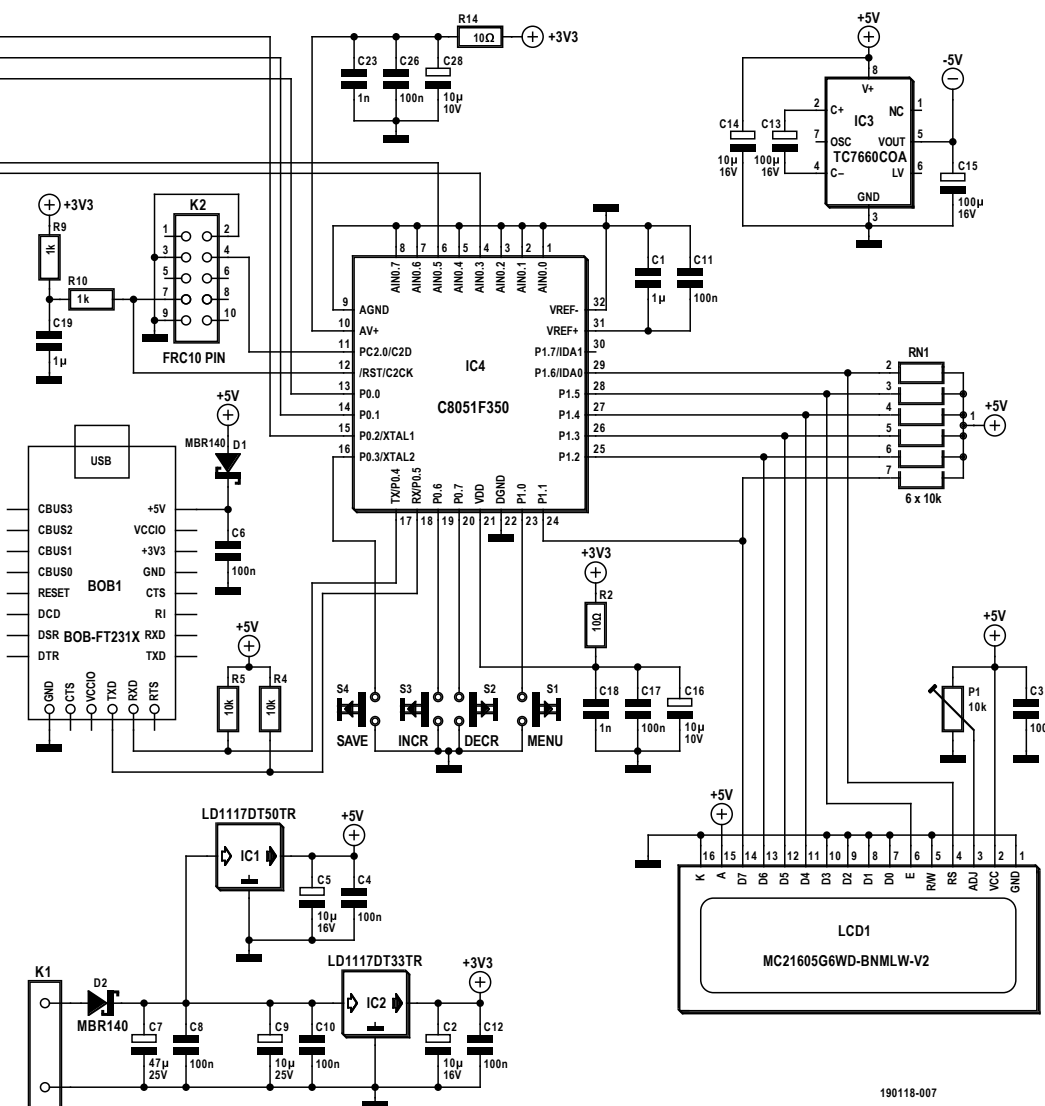


Figure 3: Schematic of the multi-node temperature logger. The analogue input stage is on the left, the digital part on the right.

 


Figure 4: The assembled main board. Note: the board shown is version 1.0 that used the legacy FT232R BoB instead of the FT231X BoB.

Each multiplexer has eight channels, two of which are used for reference signals  $V_{\min}$  (GND) and  $V_{\max}$  ( $V_{R3}$ ). Now you finally understand why there are six RTD channels and not seven or five. These reference signals follow the same paths as the RTD signals ( $R3$ , a 0.01% tolerance resistor, is even mounted close to the RTD connectors to mimic an RTD as close as possible). Because the values of these signals are known, this allows the software to calibrate the digitizer stage and remove errors introduced by the multiplexer and current source.

The outputs of the input multiplexer are individually amplified by a factor of 13 by IC6 and IC8. The signal 'V' from Figure 2 then arrives at the microcontroller's ADC input 3 (AIN0.3), while signal 'VRW' connects to AIN0.5.

### Current source, part two

The Howland current source in the project comprises IC10, resistors R1, R20, R21 and R22.  $V^+$  from our description above is connected to GND and therefore has a value of 0 V.  $V^-$  is equal to  $-2.5$  V, produced by voltage reference IC11. R21 corresponds to R3 from the description above. The output current is:  $(0 - -2.5) / 10,000 = +250$  [ $\mu$ A].

### Power supply

Theoretically, the supply voltage for the circuit connected to K1 can be up to 15 VDC, but this will put unnecessary strain on the low-drop voltage regulators. The minimum supply voltage is 7.5 VDC, the recommended value is 9 VDC. The total current consumption is around 70 mA including the 20 mA consumed by the backlight in LCD1. (Note that the latter has a built-in current limiting resistor.) IC1 lowers the supply voltage to 5 V for most of the circuit except microcontroller IC4; IC2 creates a 3.3-volt supply for this clever part.

The analogue input stage also requires a  $-5$  V supply voltage, and this is taken care of by IC3.

### The microcontroller

Over the past years, we have seen so many Arduino-based circuits flashing by that some have come to believe that there exists only one type of 8-bit microcontroller. That this is not true is proven by our circuit with its pimped-up, 8051-based brain! Now, before turning away in disgust, be aware that almost forty years after its introduction the 8051 is still a widely used 8-bit processor. Manufactured by Silicon Labs, the C8051F350

MCU used here runs internally at 49 MHz and executes most of its instructions in one cycle, making it a pretty fast device. The C8051F350 is part of a family of four that differ only by package type and ADC resolution. The 'F350 is the largest part with a 24-bit sigma-delta ADC, eight dedicated analogue inputs, and 17 digital I/O pins. It's an analogue-oriented controller with built-in digital filters and two 8-bit DACs. In this project we do not use all its capabilities, but you may want to study the MPU further for some future project.

Although running from 3.3 volts, the C8051F350's digital I/O pins are 5 V tolerant, which is why it interfaces nicely with the 5-volt-powered peripheral circuitry (note the pull-up resistors R4 to R8 and network RN1).

A quartz crystal or resonator is not called for as the MCU has a calibrated oscillator on chip.

Four pushbuttons (S1–S4) and an LCD provide the user interface. P1 sets the display contrast level; if you forget to adjust it when you power the board for the first time, the display may not show anything.

For communication with a computer, we added the option to plug a USB-to-

TTL-serial converter onto the board. We used our own breakout board, but it is also possible to connect a functionally equivalent interface. Please note that the photographs in this article show a prototype which used Elektor's (golden oldie) FT232R BoB, no. 110553. Since then it got replaced by our new FT231X BoB no. 180537 which is compatible with the *de facto* standard of 'FTDI' USB-to-serial cables.

### Software dealings

At the time of writing the kind people of Silicon Labs still handed out free licenses for Keil  $\mu$ Vision5 so people who develop software for the C8051 devices in C can do this in a comfortable way. When you request such a license it seems to be valid for just one month, but once installed in the IDE it becomes a permanent license. Of course, we have explored this avenue, and everything went fine — yet you never know when they decide to stop doing this and so we ported our software to SDCC, the open source compiler for 8051 and PIC devices.

SDCC does not work with projects and does not make use of any other GCC-based tool. Our project therefore is just a bunch of files in a folder together with a batch file to compile them.

As with every C program, the visible part starts in the function `main`. The first thing to do here is to switch off the watchdog timer; you can always switch it back on later when you are ready for it. (Note that the Keil compiler does this in the runtime (CRT) startup file so you don't notice it. We found that out the hard way.)

After initializing the MCU's peripherals — 1 ms system tick timer, UART running at 9600 baud, etc. — the program performs a calibration of the ADC.

This is a pretty neat feature of the MCU as it allows us to calibrate away many of the imperfections of our analogue front end. After calibration, converting  $V_{\max}$  — the voltage over 0.01% resistor R3 — will read as `0xffff` (24-bit maximum value) while  $V_{\min}$  (GND) will produce a reading of `0`. The ADC applies

the corrections in hardware; nothing to do for us in software.

### A word on sampling

The rest of the time `main` will spin in an endless loop, scanning for key presses and updating the display when needed. Every second a sample is taken from a channel, converted to a value in degrees Celsius or Fahrenheit and printed to the screen. A second later the next channel in line is updated. In the background the ADC runs at a faster rate of nearly 18.7 Hz. This higher speed is necessary for two reasons. First, to measure one RTD two voltages ('V' and 'VRW') have to be converted as the RTD value must be compensated for the voltage over the connecting wires. Second, the ADC has a built-in low-pass filter that needs three samples to calculate an output value. Therefore, at least six samples are required for one RTD measurement, which corresponds to 320 ms. By reducing the display time to 1 Hz, the system has enough slack to sample and filter comfortably.

### Lookup table

Samples must be converted to temperature values and this is done with the help of a lookup table. Pt100 conversion tables can be found on the Internet and we compiled one from  $-240$  °C to  $+850$  °C with a 10-degree step size. Below  $-240$  °C things become highly inaccurate and so we limited the display to  $-260$  °C (which actually means Underflow). For sim-

ilar reasons the upper limit was fixed at  $+850$  °C.

Of course, most ADC readings will be in between two table values, hence linear interpolation is used to estimate the temperature. If more precise conversions are desired, it is possible to make the lookup table's step size smaller, as long as it fits in memory (of which there is not a lot). If the table becomes really large and unwieldy, you might want to implement a more efficient search algorithm than the linear search we used or use a polynomial approximation.

### Construction

Even though the project uses mostly SMT parts, assembling the PCB should not be too difficult. Start by mounting 2-terminal parts like resistors and ceramic capacitors and then continue with the taller parts. Respect and verify the polarity of polarized parts like diodes and electrolytic capacitors.


It is always a good idea to build and test the power supply (D2, IC1 and IC2 and the capacitors around them) before mounting the other parts.

Make sure to use resistors with 1% tolerance in the input stage, except R3 which must have a tolerance of 0.01%. To create a real good current source, you might want to use 0.1% tolerance resistors for R1, R20, R21 & R22.

Depending on if and how you mount the USB-serial interface, you may want to use extra-tall connectors for the display as it is mounted over the serial BoB.
 
### Loading the firmware

Connector K2 is used for programming the firmware into the MCU. This connector follows the official Silicon Labs 2-wire C2 Programming/Debug-



ging Interface Standard so connecting a C2-compatible programmer should be easy. Less easy, on the other hand, is getting your hands on such a programmer, which is why we rolled our own. The free download on the support page for this article [3] includes an Arduino sketch that transforms any Arduino-Uno-compatible board into a C2 programmer. You can also find it on GitHub [2]. The MCU's 5 V-tolerant pins allow us to do this with impunity.

Connect Arduino pin A0 to K2 pin 7 ('C2CK'), Arduino pin A1 to K2 pin 4 ('C2D'), and Arduino GND to K2 pin 2.

Connect the Arduino to the computer before powering the board and all should be fine.

A Python 3 script, also included in the download, permits uploading Intel HEX files to the home-brew programmer. This script requires pySerial.

### Using the system

There are two firmwares for this project, one with debugging options ('d' suffix) and one with fewer options. The main UI functions are the same for both.

- 'Menu' (S1): press this button to

enter the settings "page". On this page you can toggle the temperature unit between Celsius and Fahrenheit by pressing S1 again. With the keys 'Decr' (S2) and 'Incr' (S3) you can adjust the display refresh value from one second to one minute. When done, you can either press 'Save' (S4) to store the new settings in non-volatile memory or let the page time out. When the page times out the new settings will be used until the next change or a power cycle.

- 'Save' (S4): press to recalibrate the system.



## COMPONENT LIST

### Resistors (0805, 1%)

R4,R5,R6,R7,R8 = 10kΩ  
 R1,R20,R21,R22 = 10kΩ 0.1%  
 R2,R14 = 10Ω  
 R3 = 470Ω 0.01%  
 R9,R10,R11,R12,R13,R15,R17,R18,R23 = 1kΩ  
 R16,R19 = 12kΩ  
 P1 = trimmer 10kΩ  
 RN1 = resistor network, 6×10kΩ

### Capacitors (0805)

C1,C19 = 1μF  
 C2,C5,C9,C14,C16,C28 = 10μF, 16V, Case-A  
 C3,C4,C6,C8,C10,C11,C12,C17,C20,C21,C22,C24,C25,C26,C27,C29,C30,C31,C32,C33,C34,C35,C36,C38,C39,C40,C41 = 0.1μF  
 C7 = 47μF, 25V, 6.3mm diam.

C13,C15 = 100μF, 16V, Case-C  
 C18,C23,C37 = 1nF

### Semiconductors

D1,D2 = MBR140SFT1G  
 IC1 = LD1117DT50TR  
 IC2 = LD1117DT33TR  
 IC3 = TC7660EOA  
 IC4 = C8051F350-GQ, LQFP32  
 IC5,IC7,IC9 = 4051, SOIC16  
 IC6,IC8,IC10 = OP07CD  
 IC11 = LM336M-2.5

### Miscellaneous

K1 = 2-way wire-to-board terminal block, 3.5mm pitch  
 K2 = 10-pin, 2-row pinheader, 2.54mm pitch

K3-K8 = 3-way wire-to-board terminal block, 3.5mm pitch


LCD1 = Alphanumeric LCD, 2 lines, 16 characters, 5V with backlight

S1-S4 = Tactile switch, 6×6.2mm, SMD

BOB1 = USB/Serial Bridge/BOB with suitable connectors

16-way pin socket + pinheader, 2.54mm pitch for LCD1

Elektor PCB # 130548-1

 

The debug firmware adds to this:


- 'Decr' (S2): pressing this key during startup and keeping it pressed until the splash screens have passed will skip ADC calibration at startup. Use 'Save' (S4) to calibrate when you want to.
- 'Decr' (S2) and 'Incr' (S3): pressing these keys at the same time will open the debug page where you can see raw 16-bit ADC values for both the signals 'V' (RTD) and 'VRW' (Wire). Pressing 'Incr' will select the next channel. Press 'Save' (S4) to return to normal mode.

### Data logging

Plug BOB1 on the board (or use another USB-to-serial converter, the connections are compatible with an 'FTDI' cable) and connect it to a free USB port on a PC. The latter should detect it as a serial port. Launch a terminal program and configure it for 9600 baud, eight data bits, no parity and one stop bit (9600n81). As soon as the board is powered, it will start sending comma-separated values (CSV) in human-readable ASCII format. Most
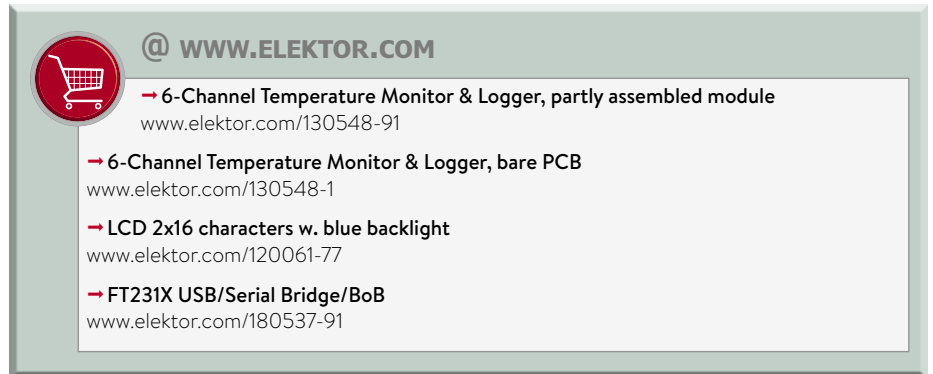
### Web Links

- [1] Project at Elektor Labs: [www.elektormagazine.com/labs/6-channel-temperature-monitor-logger](http://www.elektormagazine.com/labs/6-channel-temperature-monitor-logger)
- [2] C2 Programmer at GitHub: [https://github.com/ElektorLabs/ElektorLabs\\_Tools](https://github.com/ElektorLabs/ElektorLabs_Tools)
- [3] Web page for this project: [www.elektormagazine.com/190118-01](http://www.elektormagazine.com/190118-01)



@ WWW.ELEKTOR.COM

- 6-Channel Temperature Monitor & Logger, partly assembled module [www.elektor.com/130548-91](http://www.elektor.com/130548-91)
- 6-Channel Temperature Monitor & Logger, bare PCB [www.elektor.com/130548-1](http://www.elektor.com/130548-1)
- LCD 2x16 characters w. blue backlight [www.elektor.com/120061-77](http://www.elektor.com/120061-77)
- FT231X USB/Serial Bridge/BoB [www.elektor.com/180537-91](http://www.elektor.com/180537-91)

serial port terminal programs will allow you to record the data to a file so it can be processed further in for instance a spreadsheet. ◀

(190118-01)

Advertisement



**Post your ideas and electronics projects all sizes/all levels/all sorts, at [www.elektor-labs.com](http://www.elektor-labs.com) and become famous!**

**Elektor Labs: [www.elektor-labs.com](http://www.elektor-labs.com)**  
Design, Build, Share... Electronics!

The background image shows a hand holding a green PCB with a red component. The website interface includes a search bar, a 'Create project' button, and a 'LATEST COMMENTS' section with user avatars and text.